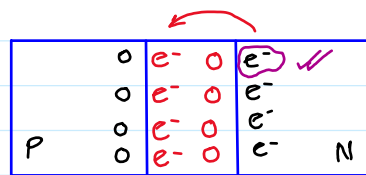



Electronics | Lecture # 02 | ECAT | MDCAT | Bilal Zia

DIODE



depletion region $\Rightarrow \Delta V$

BIASING

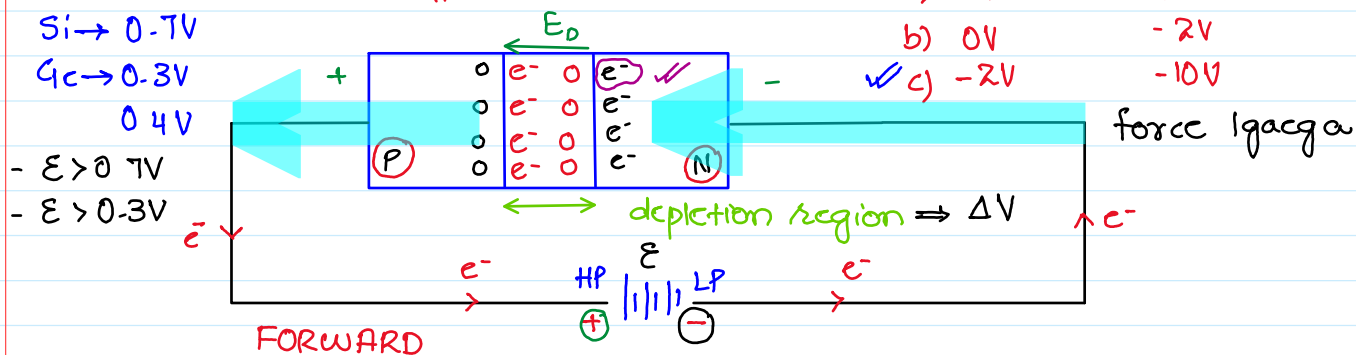


I = flow

Allow

depletion layer: THIN ≈ 0


Short Ckt

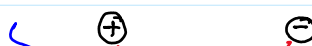

$R=0$

$R=0 \Rightarrow$ SHORT CKT path

REVERSE BIASING.

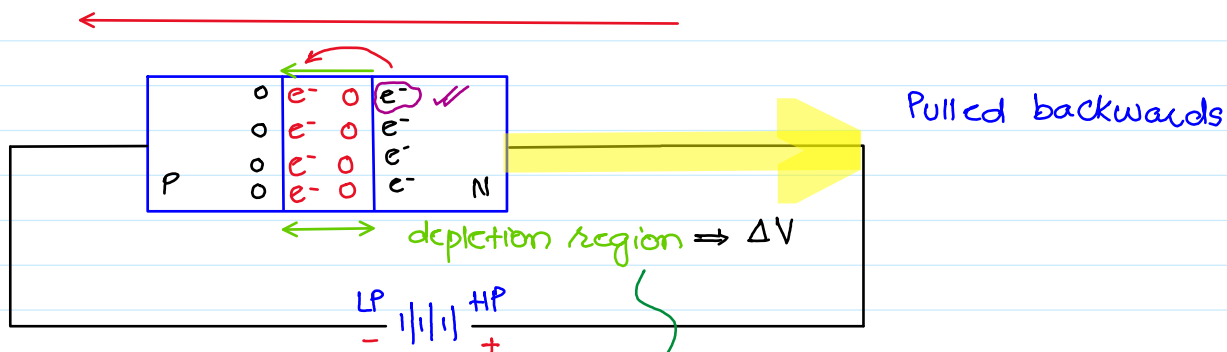

I = donot flow

Block


diode: donot allow


Open Ckt ($R: \infty$)

depletion layer: width $\uparrow \uparrow$

DIODE: ONE WAY SWITCH

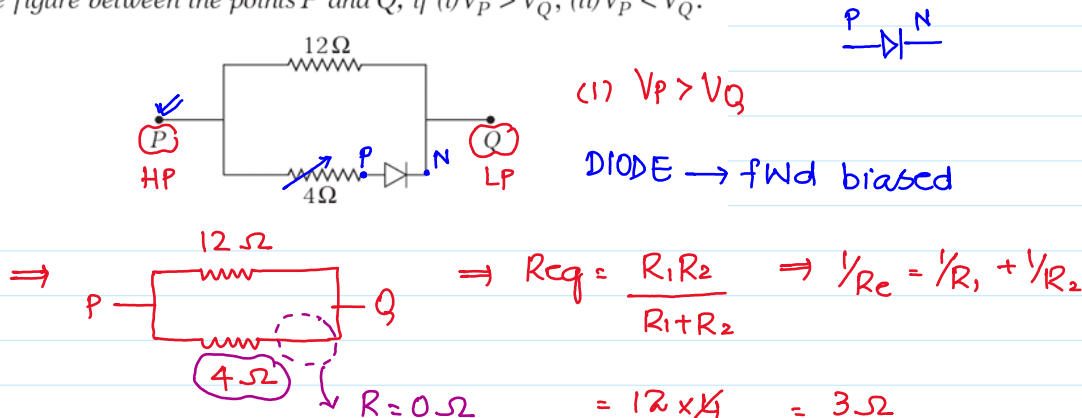
Find the net resistance of the network shown in the figure between the points P and Q, if (i) $V_P > V_Q$, (ii) $V_P < V_Q$.




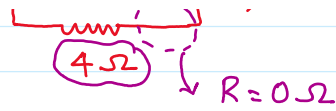


$$R_1, R_2 = \frac{12 \times 4}{12 + 4} = 3\Omega$$

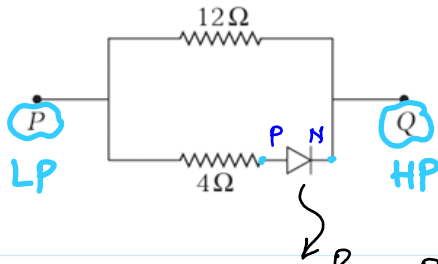Find the net resistance of the network shown in the figure between the points P and Q, if (i) $V_P > V_Q$, (ii) $V_P < V_Q$.



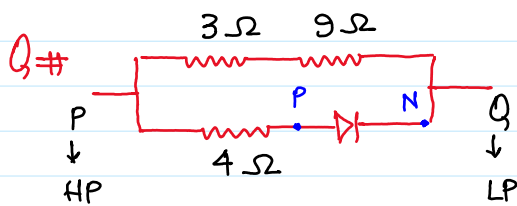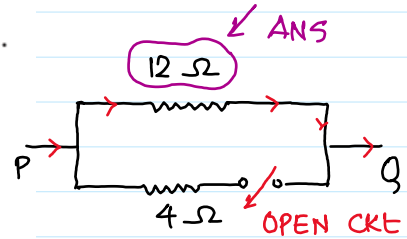REV. BIASED $\Rightarrow$ diode $\Rightarrow$ OC $\Rightarrow R: \infty$





① $V_P > V_Q$ ② $V_P < V_Q$



TOTAL resistance

① $V_P > V_Q \Rightarrow$ diode: FWB $\rightarrow R=0$

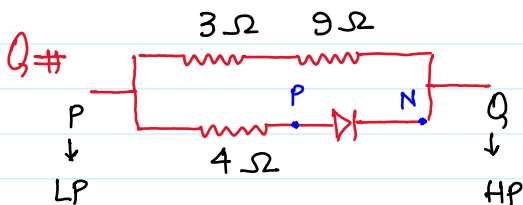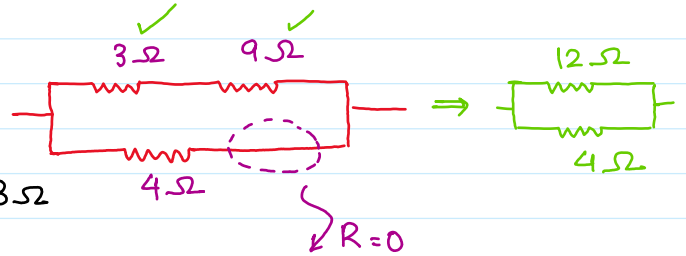
$$\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} ; R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = 3\Omega$$



① $V_A > V_B$ ② $V_A < V_B$

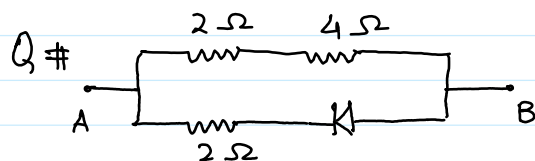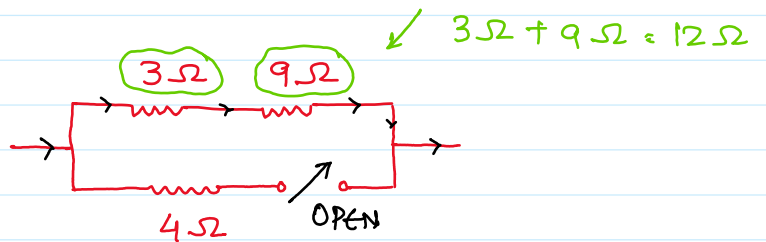


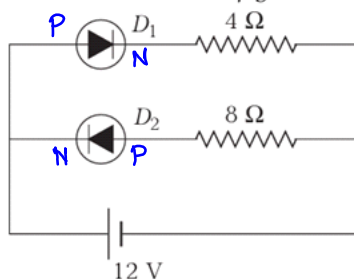Find current passing through 4Ω and 8Ω resistance in the circuit shown in figure.




$D_1 \rightarrow$ FWB ; $D_2 \rightarrow$ RWB

$8\Omega \rightarrow$ OA

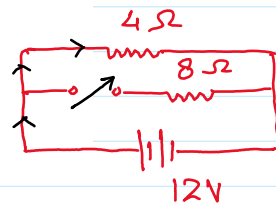

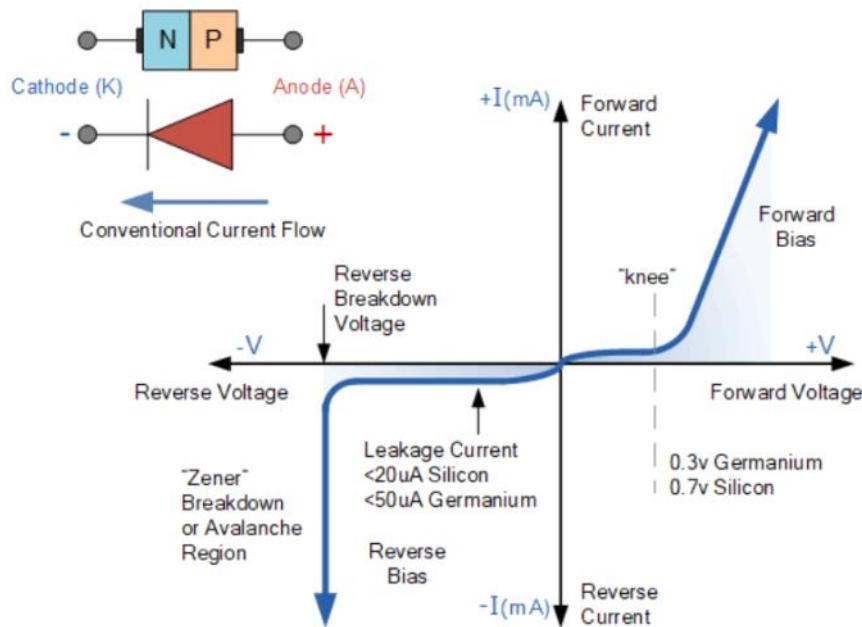
$$4\Omega = \frac{V}{I} ; I = \frac{V}{R} = \frac{12}{4} = 3A$$



$V_A > P_B$

$V = IR \rightarrow$ st line
 $V \& I \rightarrow$ OHMIC cond.


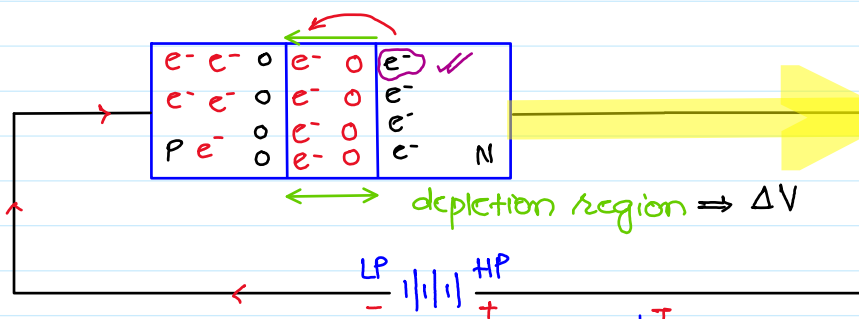
diode $\rightarrow$ N. OHMIC
 $\rightarrow$ Non. linear



Bi-Directional I

RECTIFICATION



AC $\rightarrow$ DC

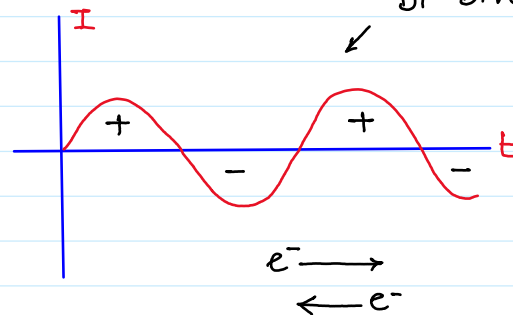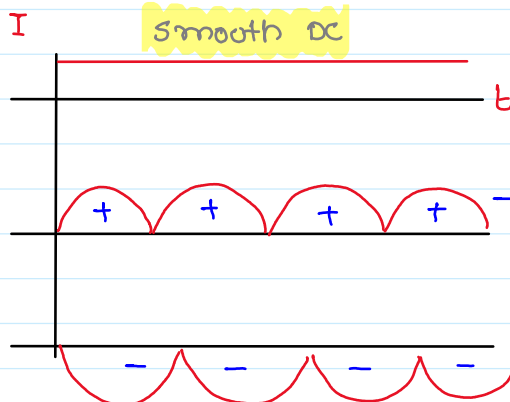



$\rightarrow$ UNI-direction

Smooth DC

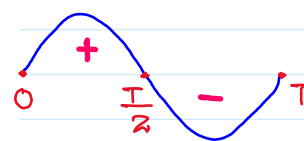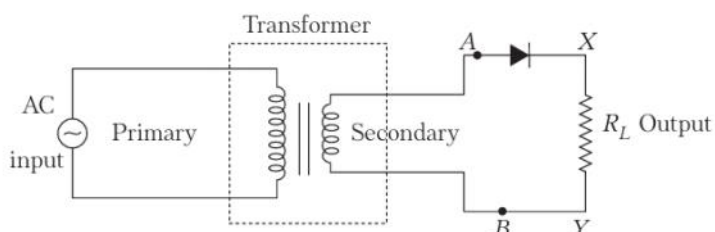A simple rectifier circuit called the half-wave rectifier, using only one diode is shown in figure. The AC voltage to be rectified is connected to the primary coil of a step-down transformer. Secondary coil is connected to the diode through resistor R_L across which, output is obtained.




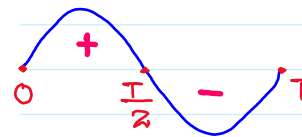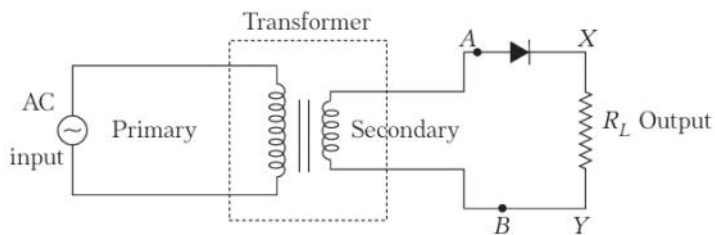A simple rectifier circuit called the half-wave rectifier, using only one diode is shown in figure. The AC voltage to be rectified is connected to the primary coil of a step-down transformer. Secondary coil is connected to the diode through resistor R_L across which, output is obtained.




$0 \rightarrow T/2$: FIRST HALF CYCLE

$T/2 \rightarrow T$: SECOND HALF CYCLE


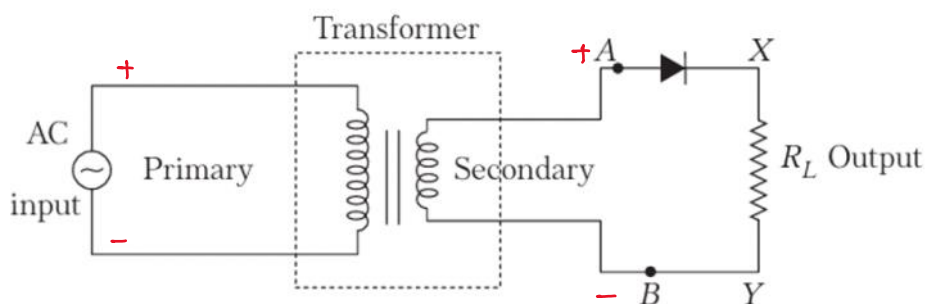


$0 \rightarrow T/2 \Rightarrow$ FwB
 $\Rightarrow$ I. flow

$x \rightarrow 3x$

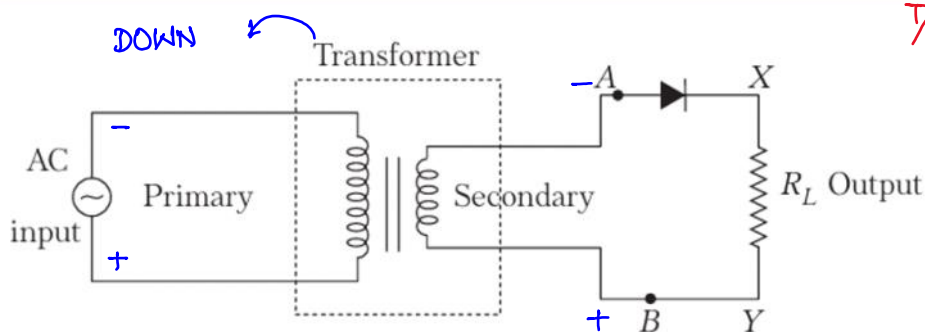

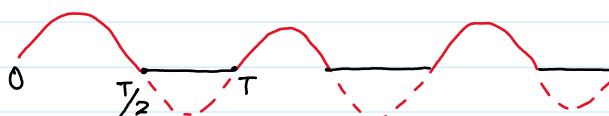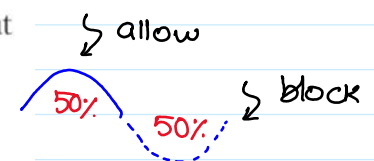
$T/2 \rightarrow T \Rightarrow$ Rwb
 $\Rightarrow I = 0$



KCL $\rightarrow$ $4A \rightarrow 2A$
 $E = VI t$
 50% $\leftarrow$ 50%

Working

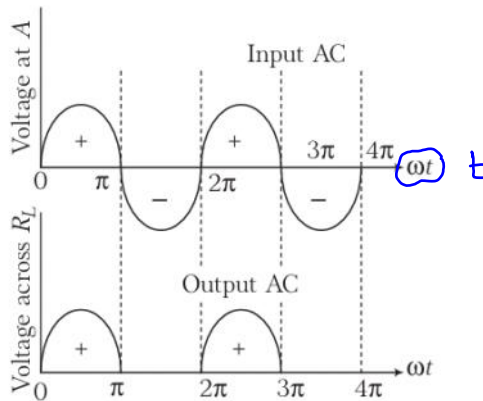During positive half cycle of the input AC (i.e. $V_A > 0$), the $p-n$ junction is in forward biased. Thus, the resistance in $p-n$ junction becomes low and current flows. Hence, we get output in the load.




NATIONAL MDCAT $\rightsquigarrow$ 2021

Ripple frequency $\rightsquigarrow$ 50 rps



Wohe hogy jo source ke "freq"

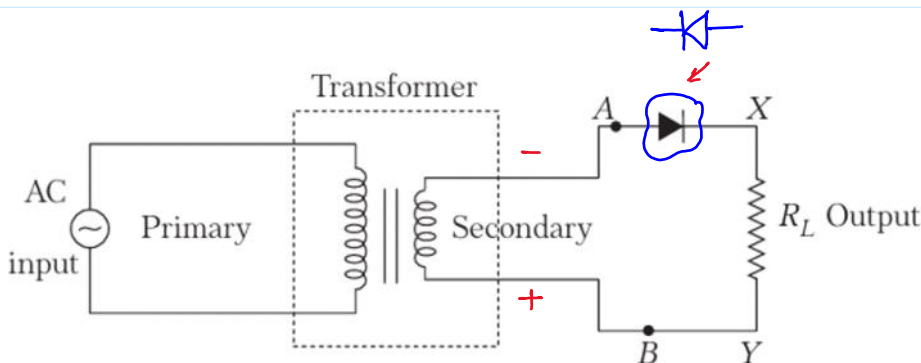AC $\rightarrow$ 50Hz $\rightarrow$ 50 cyc/sec




(i) Centre tap full wave rectifier




Figure shows a circuit which is used in full wave rectification. Two diodes are used for this purpose.

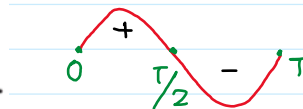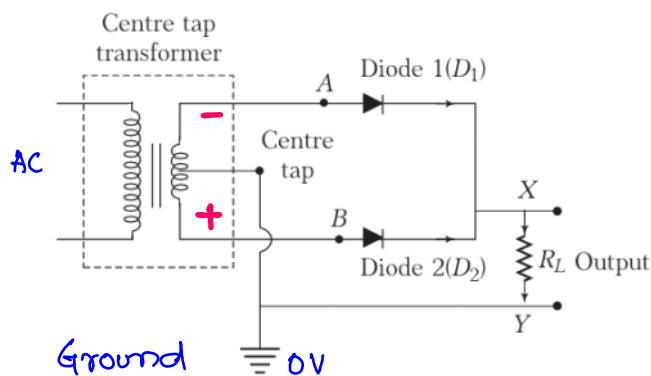


$0 - T/2 \rightarrow$ FIRST HALF CYCLE

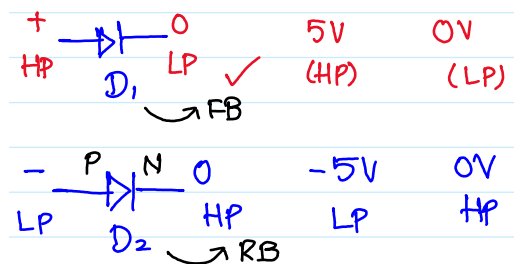


$T/2 - T \rightarrow$

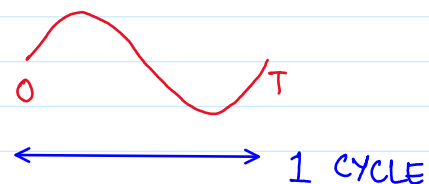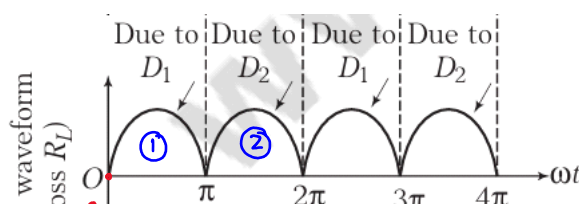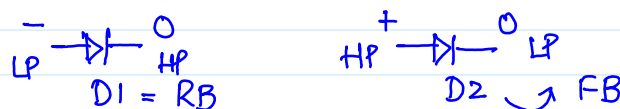

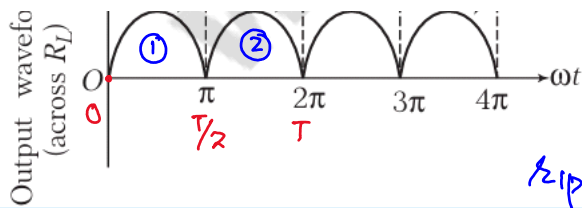

1 CYCLE
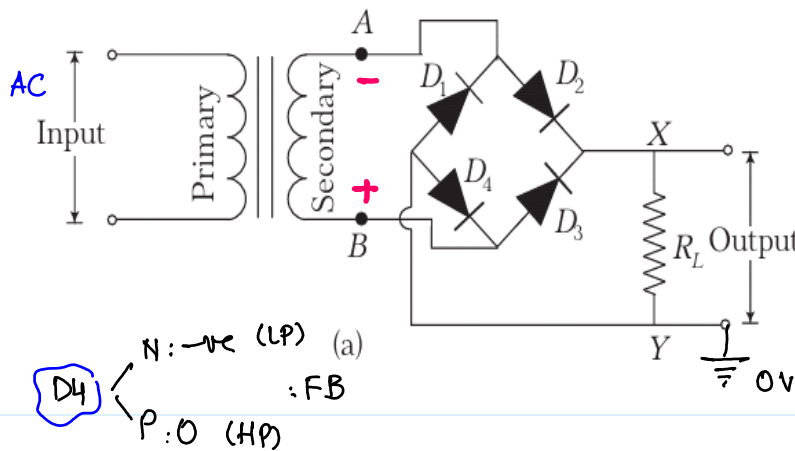
$$\text{Ripple freq} = 2 \times \text{source freq}$$



0 → T/2

D1

N: + HP

P: 0 LP

: RB

D3

N: 0 (HP)

P: -ve (LP)


: RB

D2

N: 0 (LP)

P: + (HP)

: FB

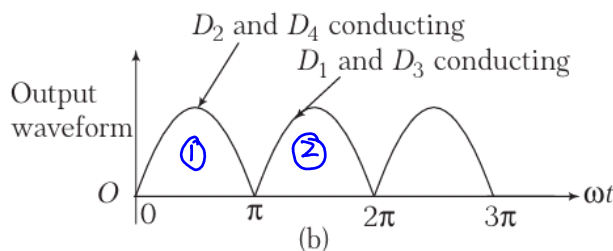

In a full wave rectifier circuit operating from 100 Hz mains frequency, what is the fundamental frequency in the ripple?

$$\Rightarrow 2 \times 100$$

$$\Rightarrow 200 \text{ Hz}$$

ripple

100 Hz

A reverse-biased diode is

- (a) -6 V -3 V
- (b) 3 V 0 V
- (c) 0 V -2 V
- (d) 2 V -3 V

Number of electrons in the valence shell of a semiconductor is

- (a) 1 (b) 2 (c) 3 (d) 4

In the circuit given below, the value of the current is

- (a) zero (b) 10^{-2} A (c) 10^2 A (d) 10^{-3} A




$$\text{HINT } I = \frac{V}{R} = \frac{\text{Pot DIFF}}{R}$$

$$= \frac{(+4) - (+1)}{300}$$


- (a) zero (b) 10^{-2} A (c) 10^2 A (d) 10^{-3} A

$$= \frac{(+4) - (+1)}{300}$$

The current in the circuit will be

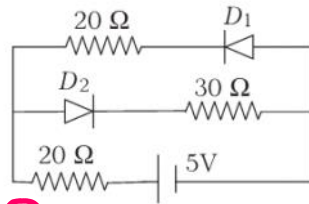

HINT $D1$ RB and $D2$: FB

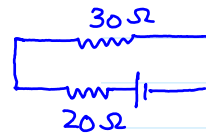


SERIES CKT
 $\Rightarrow I = \frac{V}{R}$


$$R_{eq} = 20 + 30 = 50\Omega$$

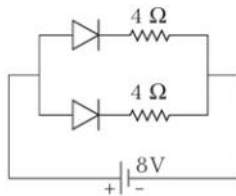- (a) $(5/40)$ A (b) $(5/50)$ A (c) $(5/10)$ A (d) $(5/20)$ A

Currents flowing in each of the circuits A and B respectively are





(Circuit A)

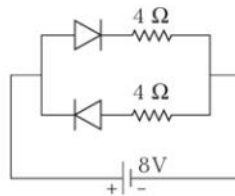


(Circuit B)

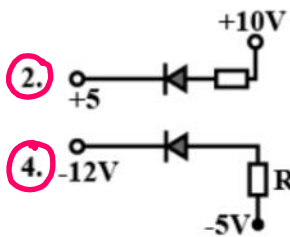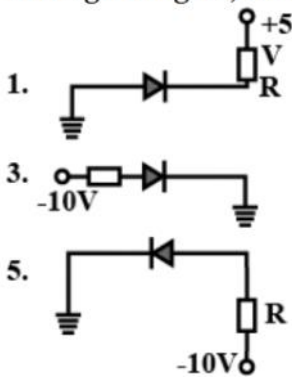- (a) 1 A, 2 A (b) 2 A, 1 A
(c) 4 A, 2 A (d) 2 A, 4 A

In the given figure, which of the diodes are forward biased?





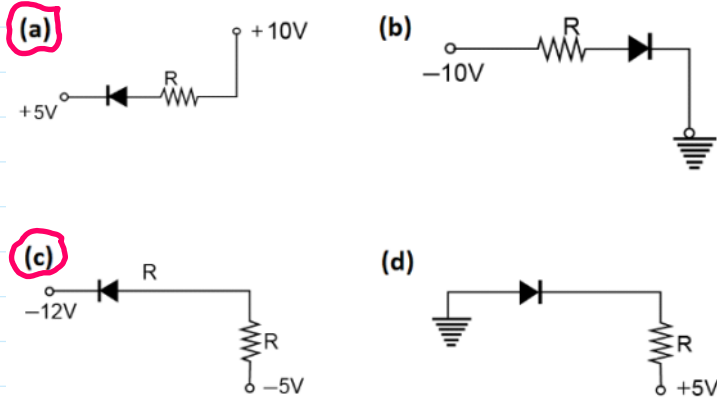In the following figure, the diodes which are forward biased, are



- A. (a), (b) and (d)
- B. (c) and (a)
- C. (b) and (d)
- D. (c) only

Out of the following, which one is a forward biased diode?

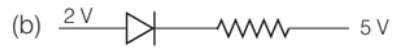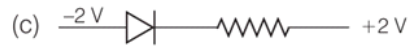- (a) 
- (b) 
- (c) 
- (d) 